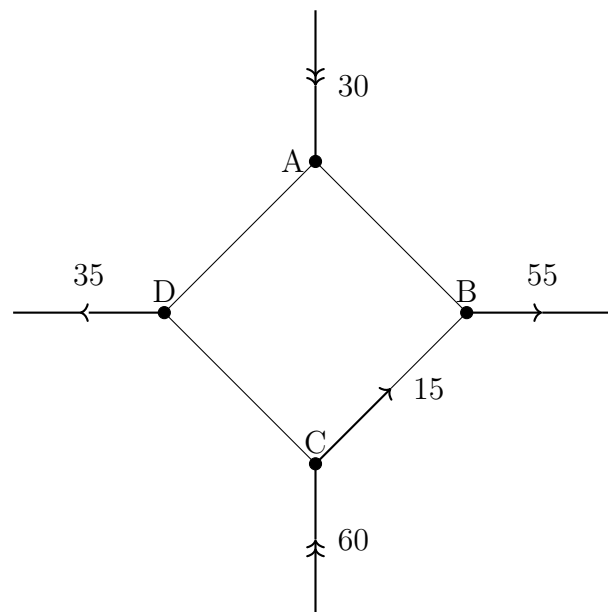


# Lecture 1 (section 1.9)

## Applications of linear systems

$\Rightarrow$  Consider a network flow with 4 nodes: A,B,C,D (can represent the **flow** of information, objects — wifi-traffic, water,cars, $\dots$ )




$\Rightarrow$  A flow rates into nodes are given


$\Rightarrow$  Flow rate along CB edge is specified

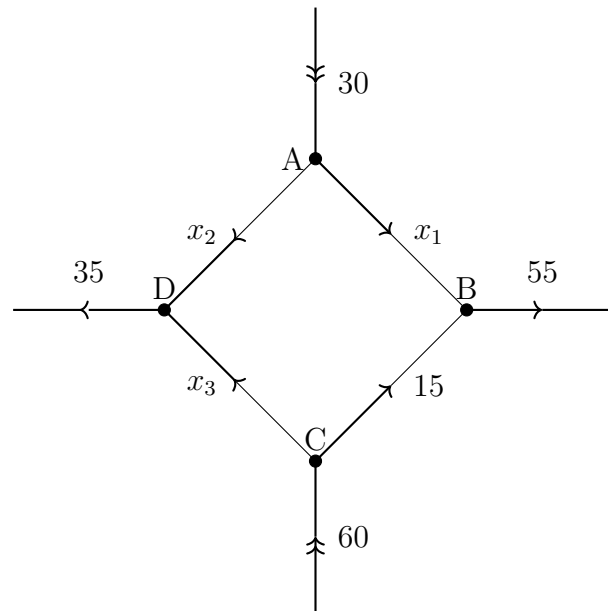**Problem:** find the remaining rates through each edge

Basic principle: flow conservation at each node



- Node A:

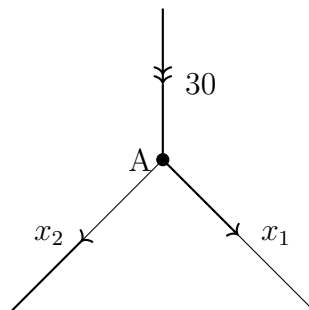

$$\underbrace{30}_{\text{"in"}} = \underbrace{x_1 + x_2}_{\text{"out"}}$$

- Node B:

$$x_1 + 15 = 55$$

- Node C:

$$60 = x_3 + 15$$

- Node D:

$$x_2 + x_3 = 35$$

Conservation laws  $\implies$  *system of linear equations*

$$\left\{ \begin{array}{ll} x_1 + x_2 = 30, & (1) \\ x_1 + 15 = 55, & (2) \\ x_3 + 15 = 60, & (3) \\ x_2 + x_3 = 35, & (4) \end{array} \right.$$

Solve problem  $\implies$  solve linear system

$$(2) : \quad x_1 = 55 - 15 = 40$$

$$(3) : \quad x_3 = 60 - 15 = 45$$

$$(1) : \quad x_2 = 30 - x_1 = 30 - 40 = -10 \quad (\text{reversed direction})$$


$$(4) : \quad \text{DOES NOT CARRY ANY NEW INFORMATION}$$

(4) is a *constraint*:

$$x_2 + x_3 = (-10) + 45 = 35 \quad \stackrel{?}{=} \quad 35 \quad (\text{eq.4})$$

$\implies$  Problem is consistent, there is a unique solution


Why consistent?

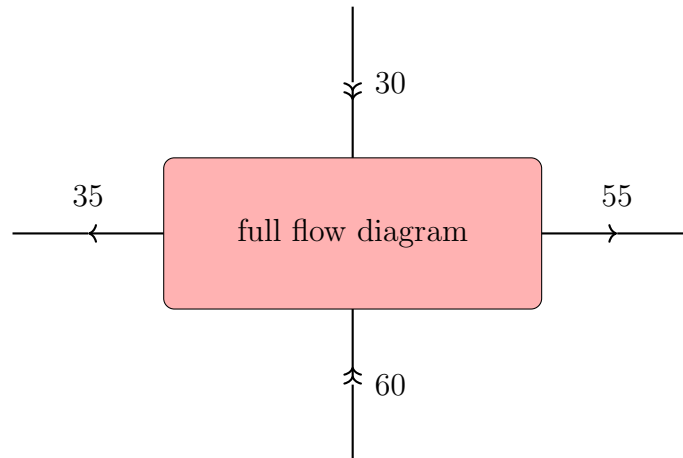

$\Rightarrow$  Because there is conservation at any node, there must be conservation for the whole network

"IN"		"OUT"
$30 + 60$		$35 + 55$
$\parallel$		$\parallel$
$90$	$\checkmark$ $\equiv$	$90$

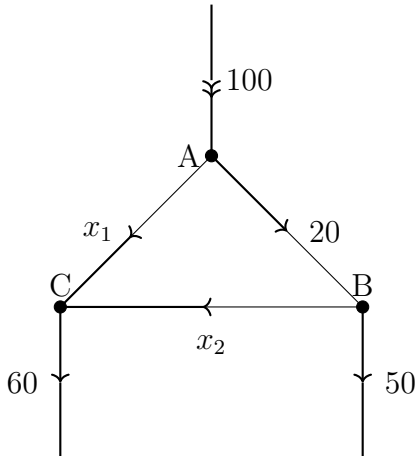Solution to linear system does not always exist:



$$\text{node A : } 100 = x_1 + 20 \quad \longrightarrow \quad x_1 = 80$$

$$\text{node B : } 20 = x_2 + 50 \quad \longrightarrow \quad x_2 = -30$$

$$\text{node C : } x_1 + x_2 = 60 \quad \longrightarrow \quad 80 + (-30) = +50 \neq 60$$

Reason:

"IN"


100

$\neq$

"OUT"

$60 + 50 = 110$

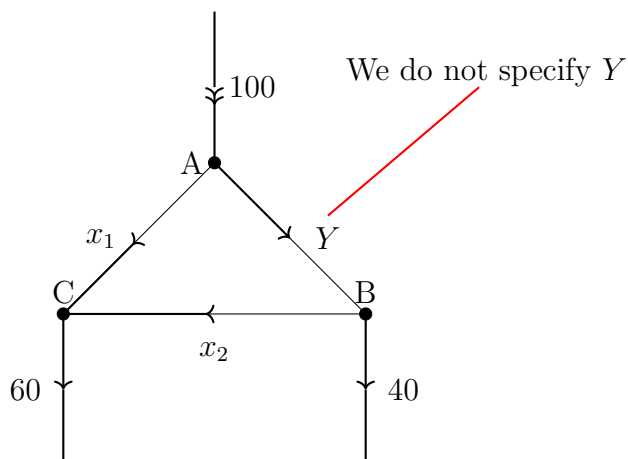Solution to linear system is not always unique:



$$\text{node A : } 100 = x_1 + Y \quad \longrightarrow \quad x_1 = 100 - Y$$

$$\text{node B : } Y = x_2 + 40 \quad \longrightarrow \quad x_2 = Y - 40$$

$$\text{node C : } x_1 + x_2 = (100 - Y) + (Y - 40) = 60 \quad \longrightarrow \quad \checkmark \equiv 60$$

$\implies$  True for any  $Y$

Consistent?

"IN"

$$100$$

=

"OUT"


$$60 + 40 = 100$$

$\implies$  In the course we study when the system of linear equations is consistent, and when there is a unique solution


$\implies$  In previous example setting  $Y = 20$  gives a unique solution; without specifying  $Y$  system of equations is underdetermined

## Electric circuits

⇒ Elementary electric circuit:

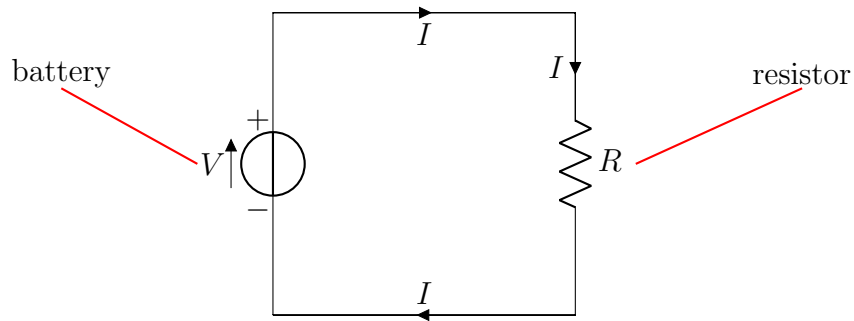

- **current**  $I$  flows from the positive pole of the battery to the negative pole
- battery is characterized by the **voltage**  $V$  (electric potential difference between the poles)
- current is characterized by a flow of positively charged particles (convention) — negatively charged particles (electrons) move in the direction opposite to that of the current
- **resistor**  $R$  reduces the *electric potential* according to **Ohm's law**:

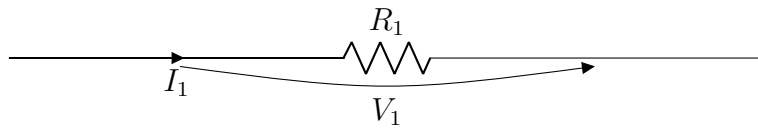


$$V_1 = R_1 \cdot I_1$$

potential drop $V_1$	resistance of the resistor $R_1$	current $I_1$
across the resistor	property of the material	through the resistor
in <b>volts</b> (V)	in <b>Ohms</b> ( $\Omega$ )	in <b>amperes</b> (A)

## Kirchoff's laws of electric circuits:


① Current conservation at each node

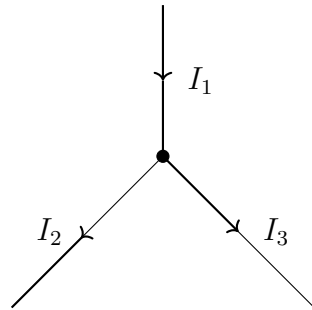

$$\underbrace{I_1}_{\text{"in"}} = \underbrace{I_2 + I_3}_{\text{"out"}}$$


② Sum of voltage rises = sum of voltage drops

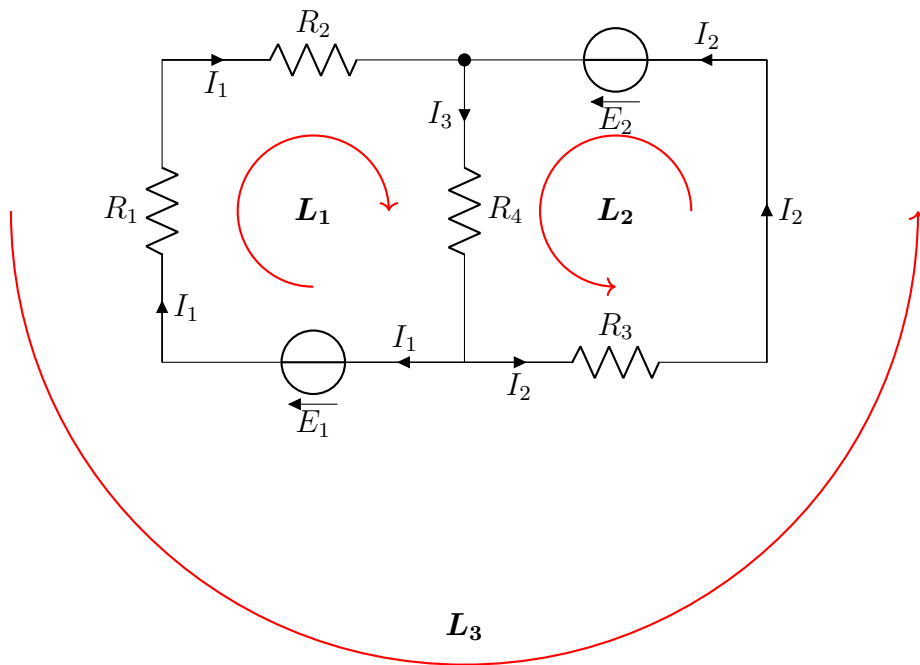$\Rightarrow$  In normal language: electric potential change is zero for any closed loop of the circuit



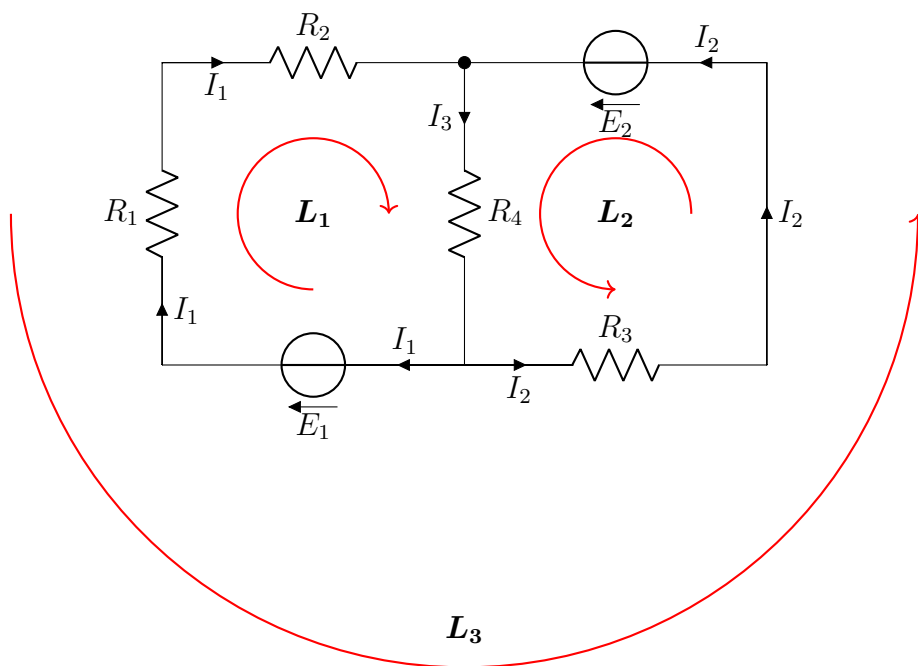$\Rightarrow$  There are 3 closed loops:  $\{\mathbf{L}_1, \mathbf{L}_2, \mathbf{L}_3\}$ ; orientation in red





$$\mathbf{L_1 :} \quad \underbrace{R_1 \cdot I_1 + R_2 \cdot I_1 + R_4 \cdot I_3}_{\text{"voltage drops"}} = \underbrace{E_1}_{\text{"voltage rises"}}$$

$$\mathbf{L_2 :} \quad \underbrace{R_4 \cdot I_3 + R_3 \cdot I_2}_{\text{"voltage drops"}} = \underbrace{E_2}_{\text{"voltage rises"}}$$

$$\mathbf{L_3 :} \quad \underbrace{R_3 \cdot I_2 + (-R_2 \cdot I_1) + (-R_1 \cdot I_1)}_{\text{"voltage drops"}} = \underbrace{(-E_1) + E_2}_{\text{"voltage rises"}}$$

$\Rightarrow$  Note **minus** signs: they appear because we are going 'against' the current direction

$\Rightarrow$  Note:

$$\mathbf{L_3 = L_2 - L_1}$$

that is, loop  $\mathbf{L_3}$  is not *independent*